

# ELC 2137 Lab 09: ALU with Input Register

Justin Woods

April 1, 2020

## Summary

The lab involved using combinational logic and sequential logic. By using sequential logic, it was possible to store values from previous inputs, as opposed to combinational logic when the output only depends on the present input. First, a D Register was created and tested using a parameter defining the bits input and output. Next an ALU was created(the combinational part of the lab), so that different arithmetic functions could be performed on the values to be input. Lastly, these modules were combined to create a Top Level ALU with a Register input.

## Results

 


Figure 1: Register Simulation Waveform and ERT

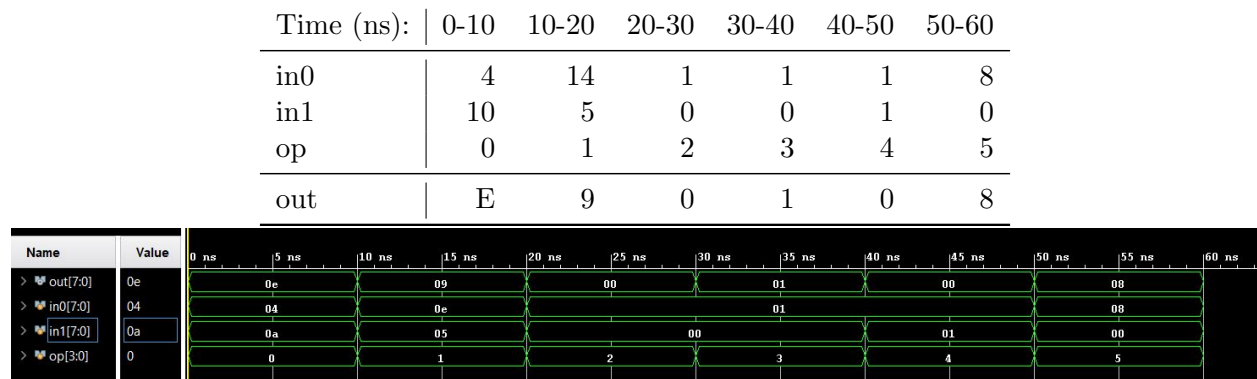


Figure 2: ALU Simulation Waveform and ERT

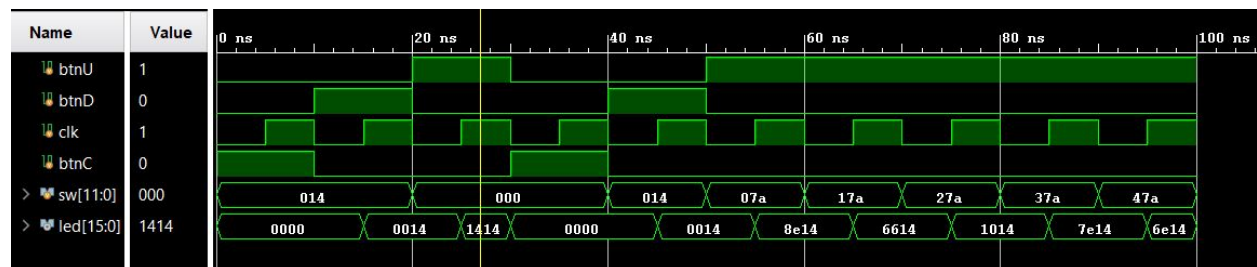


Figure 3: Top Level Waveform

## Code

Listing 1: Register Source Code

---

```
module register #(parameter N=1)
(
    input clk, rst, en, input [N-1:0] D,
    output reg [N-1:0] Q
);

always @(posedge clk, posedge rst)
begin
    if (rst==1)
        Q <= 0 ;
    else if (en==1)
        Q <= D ;
    end
endmodule
```

---

Listing 2: Register Test

---

```
module registerTEST();

    reg [3:0] D;
    reg clk, en, rst;
    wire [3:0] Q;

    register #(.N(4)) r(.D(D), .clk(clk),
        .en(en), .rst(rst),
        .Q(Q) );

    always begin
        clk = ~clk; #5;
    end

    // this block only runs once
    initial begin
        clk=0; en=0; rst=0; D=4'h0; #7;
        rst = 1; #3;
        // reset
        D = 4'hA; en = 1; rst = 0; #10;
        D = 4'h3;    #2;
        en = 0;      #5;
        en = 1;      #3;
        D = 4'h0;    #2;
        en = 0;      #10;
        en = 1;      #2;
        D = 4'h6;    #11;
        $finish;
    end
endmodule
```

---

Listing 3: ALU Source Code

---

```

module alu #(parameter N=8)
(
    output reg[N-1:0] out,
    input [N-1:0] in0,
    input [N-1:0] in1,
    input [3:0] op
);

    // Local parameters
    parameter ADD =0;
    parameter SUB =1;
    parameter AND =2;
    parameter OR  =3;
    parameter XOR =4;

    always @*
    begin
        case(op)
            ADD: out = in0 + in1;
            SUB: out = in0 - in1;
            AND: out = in0 & in1;
            OR:  out = in0 | in1;
            XOR: out = in0 ^ in1;
            default: out = in0;
        endcase
    end
endmodule

```

---

Listing 4: ALU Test

---

```

module aluTEST();

    wire[7:0] out;
    reg [7:0] in0, in1;
    reg [3:0] op;

    alu #(N(8)) a(.in0(in0), .in1(in1), .op(op),
        .out(out) );

    initial begin
        op = 0; in0 = 4; in1 = 10; #10
        op = 1; in0 = 14; in1 = 5; #10
        op = 2; in0 = 1; in1 = 0; #10
        op = 3; in0 = 1; in1 = 0; #10
        op = 4; in0 = 1; in1 = 1; #10
        op = 5; in0 = 8; in1 = 0; #10
        $finish;
    end
endmodule

```

---

Listing 5: Top Level Source Code

---

```
module top_lab9(  
    input btnU, btnD, clk, btnC,  
    input [15:0]sw,  
    output [15:0] led  
);  
  
    wire [7:0]reg1out, a1out, reg2out;  
  
    register #(N(8)) reg1 (.D(sw[7:0]), .clk(clk),  
        .en(btnD), .rst(btnC),  
        .Q(reg1out) );  
  
    alu #(N(8)) a1 (.in1(reg1out), .in0(sw[7:0]), .op(sw[11:8]),  
        .out(a1out) );  
  
    register #(N(8)) reg2 (.D(a1out), .clk(clk),  
        .en(btnU), .rst(btnC),  
        .Q(reg2out) );  
  
    assign led[7:0] = reg1out;  
    assign led[15:8] = reg2out;  
  
endmodule
```

---